400140

National Semiconductor

Telecommunications Databook

National Semiconductor

Introduction

Starting with the world's first commercially available integrated CMOS CODEC, National has gone on to establish its high performance, cost effective solutions as telecommunications industry standards.

Strategic investments in telecommunications products which help the world's telecom designers meet their targets has been a long-standing tradition at National Semiconductor. In addition, the philosophy of "continuous improvement" has resulted in enhanced products which feature extra latchup protection, improved transmit/receive crosstalk and improved ESD protection. Contact your local National sales office to ensure that you are receiving the very latest versions of these devices.

With unique experience in mixed analog/digital design, standards group participation, sophisticated laboratories and access to leading edge technologies, National's customers can continue to count on National for solutions to their design challenges.

Designers rely on National's proven track record of well-defined products.

This 1994 databook includes the latest offerings for both analog and digital loop technologies. There are also several new application notes and a handy selection guide. For the reader's convenience, the databook has been organized so that applications information immediately follows the supported devices.

Table of Contents

Alphanumeric Index vi
Definitions and Timing Conventions vii

Section 1 COMBO® CODEC/Filter and SLIC Devices, Software, Applications

COMBO Selection Guide 1-3
TP3040, TP3040A PCM Monolithic Filter 1-4
TP3054, TP3057 "Enhanced" Serial Interface CODEC/Filter COMBO Family 1-12
AN-370 Techniques for Designing with CODEC/Filter COMBO Circuits 1-26
TP3054-X, TP3057-X Extended Temperature "Enhanced" Serial Interface CODEC/Filter COMBO Family 1-32
TP3064, TP3067 "Enhanced" Serial Interface CMOS CODEC/Filter COMBO 1-45
TP3069 "Enhanced" Serial Interface CMOS CODEC/Filter COMBO 1-58
TP3070, TP3071, TP3070-X COMBO II Programmable PCM CODEC/Filter 1-71
AN-614 COMBO II Programmable PCM CODEC/Filter Family Application Guide 1-88
AN-795 TP3077SW HyBal Software Manual 1-107
TP3076 COMBO II Programmable PCM CODEC/Filter for ISDN and Digital Phone Applications 1-128
TP3155 Time Slot Assignment Circuit 1-145
AN-466 Improving the Performance of a High Speed PBX Backplane 1-153

Section 2 ISDN and Other Digital Loop Devices, Software, Applications

Introduction to National Semiconductor Basic Access I.C. Set 2-3
TP3410 ISDN Basic Access Echo-Cancelling 2B1Q U Transceiver 2-8
AN-913 TP3410 2B1Q U Interface Device User's Manual 2-39
TP3420A ISDN S/T Interface Device 2-73
AN-665 TP3420A S Interface (SID) User's Guide 2-103
AN-872 TP3420A Line Interface Circuit Considerations 2-145
AN-931 Interconnecting National's TP3420A SID to Motorola SCP/HDLC Devices 2-152
TP3464, TP3465 MICROWIRE Interface Device (MID) 2-157
COP842C Single-Chip microCMOS Microcontroller 2-173
HPC16400E High Performance Communications Microcontroller 2-174
ISDN Basic Rate Interface Software for the HPC16400E High Performance Data Communications Microcontroller 2-175
AN-492 "Intuitive ISDN"—An ISDN Tutorial 2-186
AN-520 Building an ISDN Terminal/Terminal Adapter 2-191
AN-664 ISDN Basic Rate Interface Terminal Equipment (TE) System Design Guide 2-199
AN-796 ISDN Basic Access Components for the Design of ISDN Peripherals 2-208
ISDN Glossary of Terms 2-218
TP3401, TP3402, TP3403 DASL Digital Adapter for Subscriber Loops 2-222
AN-509 Using the TP3401, TP3402, TP3403 ISDN PBX Transceivers 2-235
TP3404 Quad Digital Adapter for Subscriber Loops (QDASL) 2-248

Section 3 Analog Telephone Components

TP5088 DTMF Generator for Binary Data 3-3
TP5089 DTMF (Touch-Tone) Generator 3-7
TP5700A Telephone Speech Circuit 3-11

Section 4 Physical Dimensions/Appendices

AN-336 Understanding Integrated Circuit Package Power Capabilities 4-3
Physical Dimensions 4-8
Bookshelf
Distributors